

# Correction TD1 : Transformateur monophasé

## Exercice 1

1°/  $m = \frac{U_{2V}}{U_{1V}} = \frac{225}{1500} = 0,15$

2°/  $\cos\phi_V = \frac{P_{1V}}{U_{1V} I_{1V}}$   
 $I_a = I_{1V} \cos\phi_V$   
 $\cos\phi_V = \frac{300}{1500 \times 2} = 0,1$   
 $\rightarrow I_a = 2 \times 0,1 = 0,2 \text{ A}$

3°/  $P_{JV} = R_1 I_{1V}^2$        $R_1 = \frac{U_1}{I_1} = \frac{2,15}{10} = 0,215 \Omega$   
 $P_{JV} = 0,215 \times 2^2 = 0,86 \text{ W}$       essai en court-circuit  
 $P_{JV} \ll P_{1V} = P_{FV}$

4°/  $P_{FV} = \alpha \times U_1^2$   
 Lors de l'essai en court-circuit :  $P_{FVcc} = \alpha U_{1cc}^2$   
 à vide :  $P_{FV} = \alpha U_{1V}^2$

$\Rightarrow \alpha = \frac{P_{FV}}{U_{1V}^2} = \frac{300}{1500^2} = 133 \cdot 10^{-6} \text{ S}$

ce qui nous permet de calculer  $P_{FVcc}$   
 $P_{FVcc} = \alpha U_{1cc}^2 = 133 \cdot 10^{-6} \times 225^2 =$

**$P_{FVcc} = 0,0675 \text{ W}$**

autre méthode: à vide  $P_{FV} = \alpha \times U_{1V}^2$   
 en court-circuit  $P_{FVcc} = \alpha U_{1cc}^2$

$\Rightarrow \frac{P_{FVcc}}{P_{FV}} = \frac{\alpha U_{1cc}^2}{\alpha U_{1V}^2} = \left( \frac{U_{1cc}}{U_{1V}} \right)^2 \Rightarrow$


**$P_{FVcc} = P_{FV} \times \left( \frac{U_{1cc}}{U_{1V}} \right)^2$**

AN:  $P_{FVcc} = 300 \times \left( \frac{225}{1500} \right)^2 \approx 0,0675 \text{ W}$

5°/  $R_s = \frac{P_{Vcc}}{I_{2cc}^2}$  avec  $I_{2cc} = \frac{I_{1cc}}{m} = \frac{225 \cdot 150}{0,15} \text{ A}$

$R_s = \frac{225}{150^2} = 10 \text{ m}\Omega$  ;  $Z_s = \frac{m U_{1cc}}{I_{2cc}} = \frac{0,15 \times 225}{150}$

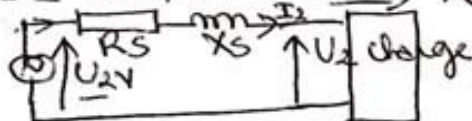$Z_s = 22,5 \text{ m}\Omega \Rightarrow X_s = \sqrt{Z_s^2 - R_s^2} = 20,15 \text{ m}\Omega$



$$6^o) \quad U_1 = 1500V;$$

$$I_2 = 200A$$

$$a) \quad \varphi_2 = (\vec{I}_2, \vec{U}_2)$$

$$\Delta U_2 \approx R_S I_2 \cos \varphi_2 + X_S I_2 \sin \varphi_2 = 0$$

$$\Rightarrow R_S I_2 \cos \varphi_2 = -X_S I_2 \sin \varphi_2$$

$$\Rightarrow R_S \cos \varphi_2 = -X_S \sin \varphi_2$$

$$\Rightarrow \frac{R_S}{X_S} = -\frac{\sin \varphi_2}{\cos \varphi_2} = -\tan \varphi_2 \Rightarrow \boxed{\tan \varphi_2 = -\frac{R_S}{X_S}}$$

$$\text{AN: } \tan \varphi_2 = -\frac{10}{20,15} = -0,496$$

$$\varphi_2 = \tan^{-1}(-0,496) = -26,38^\circ$$

il faut une charge capacitive de facteur de puissance

$$\cos \varphi_2 = \cos(-26,38) = 0,895$$

$$b) \quad \frac{\Delta U_2}{U_2} \% ?$$

$$\Delta U_2 \% = \frac{100(U_{2V} - U_2)}{U_{2V}} = \frac{\Delta U_2}{U_{2V}} \times 100$$

$$\Delta U_2 = R_S I_2 \cos \varphi_2 + X_S I_2 \sin \varphi_2$$

$$\varphi_2 = \cos^{-1}(0,895) = 36,86^\circ \Rightarrow \sin \varphi_2 = 0,6$$

$$\Delta U_2 = 10 \cdot 10^3 \times 200 \times 0,895 + 20,15 \cdot 10^3 \times 200 \times 0,6$$

$$\Delta U_2 = 4V \Rightarrow \frac{\Delta U_2}{U_{2V}} = \frac{\Delta U_2}{U_{2V}} \times 100 = \frac{4}{225} \times 100$$

$$\boxed{\Delta U_2 \% = 1,777\%}$$

$$\eta = \frac{P_2}{P_1} \quad \text{avec } P_1 = P_R + P_S + P_2$$

$$P_2 = U_2 I_2 \cos \varphi_2$$

$$U_2 = U_{2V} - \Delta U_2 = 225 - 4 = 221V$$

$$P_2 = 221 \times 200 \times 0,895 = 39360W$$

$$P_1 = 39360 + 300 + 225 = 39885W$$

$$\eta = \frac{39360}{39885} = \underline{\underline{98,54\%}}$$

### Exercice 2:

1°/  $\cos \varphi = \cos 36^\circ = 0,809$

2°/ La tension nominale d'un enroulement du stator est 400V, cette tension correspond à la tension composée du réseau  $\Rightarrow$  on couple le stator du moteur en TRIANGLE.

3°/  $J = \frac{U}{Z} = \frac{400}{4615} = 8,6 \text{ A}$

4°/  $I = J \times \sqrt{3} = 8,6 \times \sqrt{3} = 14,9 \text{ A}$

5°/  $S = U I \sqrt{3} = 400 \times 14,9 \times \sqrt{3} = 10322 \text{ W}$


6°/  $P = U I \sqrt{3} \cos \varphi = 400 \times 14,9 \times \sqrt{3} \times 0,809$   
 $P = 8350 \text{ W}$

7°/  $Q = P \times \tan \varphi = 8350 \times \tan 36 = 6066 \text{ Var}$

$(Q = \sqrt{S^2 - P^2} = \sqrt{10322^2 - 8350^2} = 6066 \text{ Var})$

exercice 3

1°/

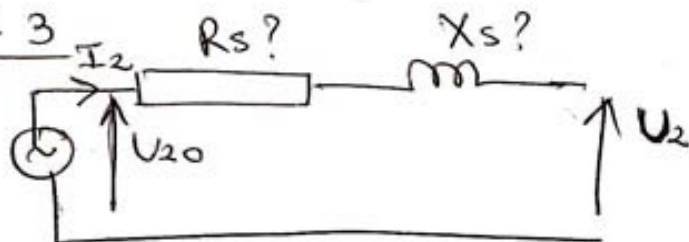

$$R_s = \frac{P_{1cc}}{I_{2cc}^2} = \frac{1000}{200^2} = 25 \text{ m}\Omega$$

$$Z_s = \frac{m U_{1cc}}{I_{2cc}} = \frac{0.045 \times 250}{200} = 56,25 \text{ m}\Omega$$

$$m = \frac{U_{20}}{U_1} = \frac{225}{5000} = 0.045$$

$$X_s = \sqrt{Z_s^2 - R_s^2} = \sqrt{56,25^2 - 25^2} = 50,39 \text{ m}\Omega$$

2°/  $U_2$  ?  $\Delta U_2 = R_s I_2 \cos \varphi_2 + X_s I_2 \sin \varphi_2$

$$\cos \varphi_2 = 0.18 \Rightarrow \varphi_2 = + \cos^{-1}(0.18) = 36,86^\circ$$

$$\sin \varphi_2 = \sin 36,86 = 0.16$$

$$\Delta U_2 = 25 \cdot 10^{-3} \times 180 \times 0.18 + 56,25 \cdot 10^{-3} \times 180 \times 0.16$$

$$\Delta U_2 = 9,675 \text{ V}$$

$$U_2 = U_{20} - \Delta U_2 = 225 - 9,675 = 215,325 \text{ V}$$

Pertes Joule:  $P_J$  ?

$$P_{1cc} = R_s I_{2cc}^2 \quad \left. \begin{array}{l} P_J = R_s I_2^2 \\ P_J = P_{1cc} \times \left(\frac{I_2}{I_{2cc}}\right)^2 = 1000 \times \left(\frac{180}{200}\right)^2 \end{array} \right\} \frac{P_J}{P_{1cc}} = \frac{R_s I_2^2}{R_s I_{2cc}^2} = \left(\frac{I_2}{I_{2cc}}\right)^2$$

$$P_J = 1000 \times \left(\frac{180}{200}\right)^2$$

$$P_J = 810 \text{ W} \quad \leftarrow \text{Pertes Joule pour } I_2 = 180 \text{ A}$$

2°/  $\eta = \frac{P_2}{P_1} = \frac{P_2}{P_2 + P_{PF} + P_J}$

$P_{PF} = P_{10} = 790 \text{ W}$   
 car tension primaire  
 identique que  
 lors del essai vide

$$P_2 = U_2 I_2 \cos \varphi_2 = 215,325 \times 180 \times 0.18 = 31006 \text{ W}$$

$$P_1 = 31006 + 790 + 810 = 32606 \text{ W}$$

$$\eta = \frac{31006}{32606} = 95\%$$

## exercice 4

$$1^{\circ} / N_1 = \frac{N_2}{m} \quad m = \frac{U_{20}}{U_{10}} = \frac{700}{10.000} = 0,07$$

$$N_1 = \frac{595}{0,07} = 8500 \text{ spires}$$

$$2^{\circ} / U_2 ? \text{ pour } I_2 = 400 \text{ A}$$

avec  $\cos \varphi_2 = 0,8$  quand  $U_1 = 10 \text{ kV}$   
 $U_2 = U_{20} - \Delta U_2$  et  $\Delta U_2 = R_s I_2 \cos \varphi_2 + X_s I_2 \sin \varphi_2$   
il faut calculer les valeurs de  $R_s$  et de  $X_s$ :

$$R_s = \frac{P_{1cc}}{I_{2cc}^2} = \frac{8000}{400^2} = 5 \text{ m}\Omega$$

$$Z_s = \frac{m U_{1cc}}{I_{2cc}} = \frac{0,07 \times 10000}{400} = 17,5 \text{ m}\Omega$$

$$X_s = \sqrt{Z_s^2 - R_s^2} = \sqrt{17,5^2 - 5^2} = 16,717 \text{ m}\Omega$$

Calcul de la chute de tension:  $\sin \varphi = \sqrt{1 - \cos^2 \varphi} = \sqrt{1 - 0,8^2} = 0,6$

$$\Delta U_2 = 5 \cdot 10^{-3} \times 400 \times 0,8 + 16,717 \cdot 10^{-3} \times 400 \times 0,6$$

$$\Delta U_2 = 56,25 \text{ V} \Rightarrow U_2 = U_{20} - \Delta U_2 = 700 - 56,25$$

$$U_2 = 643,75 \text{ V}$$

$$\text{Pour } I_2 = 200 \text{ A} \quad \Delta U_2 = R_s I_2 \cos \varphi_2 + X_s I_2 \sin \varphi_2$$

$$\Delta U_2 = 5 \cdot 10^{-3} \times 200 \times 0,8 + 16,717 \cdot 10^{-3} \times 200 \times 0,6 = 28,125 \text{ V}$$

$$P_2 = U_2 I_2 \cos \varphi_2 = (U_{20} - \Delta U_2) I_2 \cos \varphi_2 = (700 - 28,125) \times 200 \times 0,8$$

$$P_2 = 10715 \text{ kW}$$

$$P_1 = P_2 + P_F + P_J$$

$$P_J = 8000 \times \left( \frac{200}{400} \right)^2 = 2000 \text{ W}$$

$$P_F = P_{10} = 6900 \text{ W, car on a la même tension primaire}$$

$$P_1 = 10715 + 2 + 6,9 = 11614 \text{ kW}$$

$$\eta = \frac{P_2}{P_1} = \frac{10715}{11614} = 92,35\%$$

Exercice 5:


1°/

a)  $\cos \varphi_v = \frac{P_{1v}}{S_{1v}} = \frac{P_{1v}}{U_{1v} I_{1v}} = \frac{36}{220 \times 0,13} = 0,1545$

b)  $N_2 = m \times N_1 = \left(\frac{U_{2v}}{U_1}\right) \times N_1 = \frac{110 \times 500}{220} = 250 \text{ spires}$

2°/

a)

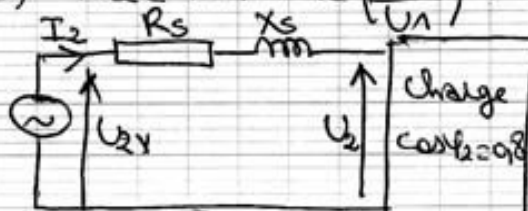

modèle équivalent de Thévenin du transformateur, vu du secondaire

$$\vec{U}_{2v} = R_s \vec{I}_2 + X_s \vec{I}_2 + \vec{U}_2$$

- calcul des éléments du modèle équivalent:

$$R_s = \frac{P_{1cc}}{I_{2cc}^2} = \frac{30}{10^2} = 300 \text{ m}\Omega$$

$$Z_s = m \frac{U_{1cc}}{I_{2cc}} = 0,15 \times \frac{10}{10} = 500 \text{ m}\Omega$$

$$X_s = \sqrt{Z_s^2 - R_s^2} = 400 \text{ m}\Omega$$

Construction de Fresnel:  $R_s I_2 = 0,13 \times 20 = 6 \text{ V}$

$$X_s I_2 = 0,14 \times 20 = 8 \text{ V}, U_{2v} = 110 \text{ V}$$

$$\varphi_2 = (\vec{I}_2, \vec{U}_2) = \cos^{-1}(0,18) = 36,86^\circ$$

Echelle: 1cm  $\rightarrow$  10cm


arc de cercle de centre O et de rayon  $U_{2v}$

- $R_s I_2 \rightarrow 0,6 \text{ cm}$
- $X_s I_2 \rightarrow 0,8 \text{ cm}$
- $U_{2v} \rightarrow 11 \text{ cm}$

$$U_2 = AB \times 10 \text{ V/cm}$$

$$U_2 = 10 \times 10 \text{ V/cm}$$

$$U_2 = 100 \text{ V}$$

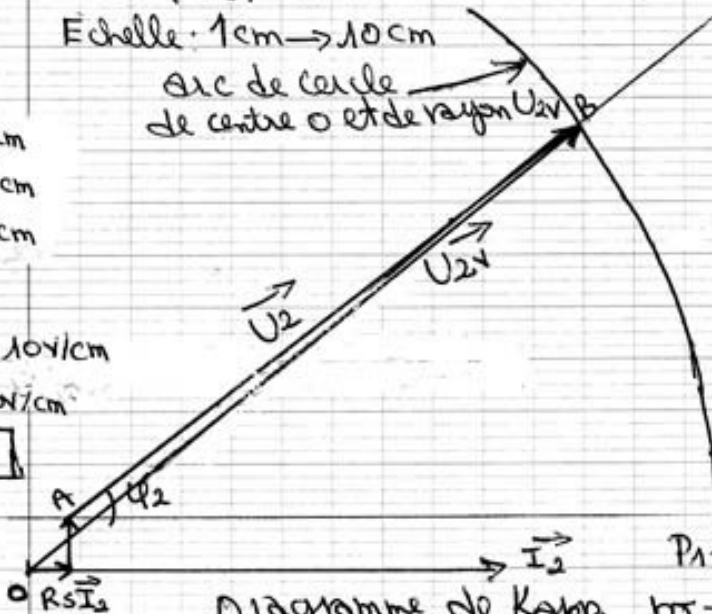

b/

$$\Delta U_2 = U_{2v} - U_2 = 110 - 100$$

$$\Delta U_2 = 10 \text{ V}$$

$$\Delta U_2 \% = \frac{\Delta U_2 \times 100}{U_{2v}}$$

$$\Delta U_2 \% = \frac{10 \times 100}{110} = 9\%$$

3°/  $P_2 = U_2 I_2 \cos \varphi_2$

$$P_2 = 100 \times 20 \times 0,8 = 1600 \text{ W}$$

$$P_1 = P_2 + P_F + P_J$$

$$P_J = P_{1cc} \left(\frac{I_2}{I_{2cc}}\right)^2 = 30 \times \left(\frac{20}{10}\right)^2$$

$$P_J = 120 \text{ W}; P_1 = 1600 + 36 + 120 = 1756 \text{ W}$$

$$\eta = \frac{P_2}{P_1} = \frac{1600}{1756} = 91,11\%$$