

Connexion TD1

2°/

2.1

$$I_{2cc} = I_{2n}$$

$$S_N = V_{2o} \cdot I_{2N} \Rightarrow I_{2N} = \frac{S}{V_{2o}}$$

$$m = \frac{I_{1cc}}{I_{2cc}} \Rightarrow \boxed{I_{2cc} = \frac{I_{1cc}}{m}} ?$$

$$\text{AN: } I_{2cc} = \frac{20}{2} = 10 \text{ A}$$

$$\underline{2.2} \quad R_S = \frac{P_{1cc}}{I_{2cc}^2} = \frac{100}{10^2} = 1 \Omega$$

$$\text{on calcule d'abord } Z_S = \frac{m V_{1cc}}{I_{2cc}}$$

$$\text{AN: } Z_S = \frac{2 \times 10}{10} = 2 \Omega$$

$$Z_S^2 = R_S^2 + X_S^2 \Rightarrow X_S = \sqrt{Z_S^2 - R_S^2} = \sqrt{2^2 - 1^2}$$

$$Z_S = \boxed{X_S = 1,73 \Omega} \Rightarrow L_S = \frac{X_S}{\omega} = \frac{1,73}{314}$$

$$\boxed{L_S = 5,516 \text{ mH}}$$

$$\underline{2.3} \quad \Delta V_2 = R_S I_2 \cos \varphi_2 + X_S I_2 \sin \varphi_2 \quad i) \varphi_2 = \frac{\pi}{6}$$

$$\Delta V_2 = 1 \times 10 \times \cos\left(\frac{\pi}{6}\right) + 1,73 \cdot 10 \sin\left(\frac{\pi}{6}\right) = 19 \text{ V}$$

$$\begin{aligned} V_{2o} &= m \times V_{1N} \\ V_{2o} &= 2 \times 80 = 160 \text{ V} \end{aligned}$$

$$\underline{2.4} \quad V_2 = V_{2o} - \Delta V_2 =$$

$$V_2 = 160 - 19 = 141 \text{ V}$$

$$P_2 = V_2 I_2 \cos \varphi_2 = 141 \times 10 \times \cos \frac{\pi}{3}$$

$$\underline{2.5} \quad \eta = \frac{P_2}{P_1}$$

$$P_2 = 1221 \text{ W}$$

$$P_1 = P_2 + P_{\text{Fert}} + P_3 = P_2 + P_{10} + P_{1cc} = 1221 + 120 + 100 =$$

$$P_1 = 1441 \text{ W} \Rightarrow \eta = 1221 / 1441 = 84,17 \%$$