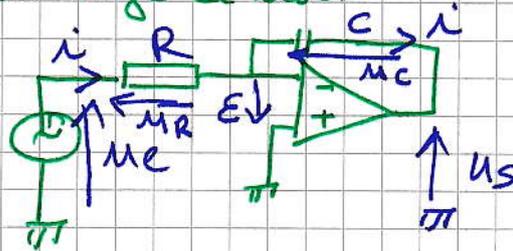


## Collection TD: Intégrales

①

1°) Montage de base:



1-1  $M_e - M_R + E = 0$   
 donc  $M_e - M_R = 0$

$M_e = R i$  ①

$M_s + M_c = 0$

$\Rightarrow M_s = -M_c$

$i = c \frac{d u_c}{dt} = -c \frac{d u_s}{dt}$  ②

② dans ①  $\Rightarrow M_e = -R c \frac{d u_s}{dt}$

ou  $\frac{d u_s}{dt} = -\frac{1}{R c} \times M_e$

1-2 à  $t=0$   $M_e(0) > 0$

$M_e = U_0 + U_{em} \cos \omega t = 0,2 + 10 \cos \omega t$

Pour  $M_e = U_0 = 0,2 \text{ V}$

$\frac{d u_s}{dt} = -\frac{1}{R c} \cdot U_0 \Rightarrow M_s(t) = -\frac{1}{R c} U_0 t + C_1$

à  $t=0$   $M_e(0) = 0 \Rightarrow M_s = 0 \Rightarrow C_1 = 0$

$\Rightarrow M_s(t) = -\frac{1}{R c} \cdot U_0 \cdot t$

$M_s = -\frac{1}{10^3 \times 100 \cdot 10^{-9}} \times 0,2 t = -200 t$

La tension  $M_s$  devient au bout d'un temps  $t_1$  l'ALI de police  $\Rightarrow -200 t_1 = -12 \Rightarrow$

$t_1 = \frac{-12}{-200} = 0,06 \text{ s}$

1.3: Pour  $u_e(t) = U_{em} \cos \omega t = 10 \cos \omega t$

$$\frac{du_s}{dt} = -\frac{1}{RC} \times U_{em} \cos \omega t$$

$$u_s(t) = -\frac{U_{em}}{RC \omega} \sin \omega t = \frac{-10 \sin \omega t}{10^{-2} \times 100 \times 10^3}$$

$$u_s(t) = -1,59 \sin \omega t$$

1.4  $u_e(t) = U_0 + U_{em} \cos \omega t$


on applique le théorème de superposition

donc  $u_s(t) = -\frac{U_0}{RC} t - \frac{U_{em}}{RC \omega} \sin \omega t$

$$u_s(t) = -200t - 1,59 \sin \omega t$$



20/

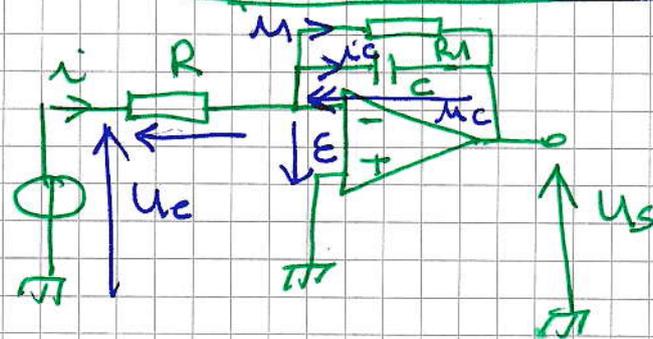

2.1

$$u_e - R i + \varepsilon = 0 \Rightarrow u_e - R i = 0$$

$$u_s + u_c + \varepsilon = 0 \Rightarrow u_s + u_c = 0$$

$$i = i_e + i_1 \Rightarrow C \frac{du_c}{dt} = -C \frac{du_s}{dt}$$

(3)

$$\dot{u} = u_c + u_1$$

$$\downarrow \quad \downarrow \quad \searrow$$

$$\frac{u_e}{R} = -C \frac{du_s}{dt} - \frac{u_s}{R_1}$$

$$R_1 C \frac{du_s}{dt} + u_s = -\frac{R_1}{R} u_e$$

2.2 Pour  $u_e = U_0$

$$R_1 C \frac{du_s}{dt} + u_s = -\frac{R_1}{R} U_0 \quad \text{ED 1<sup>re</sup> ordre}$$

$$\tau = R_1 C = 10 \times 10^3 \times 100 \cdot 10^{-9} = 0,01 \text{ s}$$

$$u_s(t) = A e^{-t/\tau} + B$$

$$\text{à } t=0 \quad u_s = -u_c = 0$$

$$u_s(0) = A + B = 0 \Rightarrow A = -B$$

$$\text{(Pour } t \rightarrow +\infty \frac{du_s}{dt} = 0 \Rightarrow u_s = -\frac{R_1 U_0}{R}) \quad B = -A = \frac{R_1 U_0}{R}$$

$$\Rightarrow u_s = -\frac{R_1}{R} U_0 (1 - e^{-t/\tau})$$

Pour  $t = 5\tau = 5 \times 0,01 = 50 \text{ ms}$

$$u_s \approx -\frac{R_1}{R} U_0 = -10 U_0 = -2 \text{ V}$$

2.3  $u_e = U_{em} \cos \omega t$

$$\text{on a } \tau \frac{du_s}{dt} + u_s = -\frac{R_1}{R} U_{em} \cos \omega t$$

$$\frac{du_s}{dt} + \frac{1}{\tau} u_s = -\frac{U_{em}}{R_1 C} \cos \omega t$$

$$\frac{du_s}{dt} = -\left( \frac{u_s}{\tau} + \frac{U_{em}}{R_1 C} \cos \omega t \right)$$

$$\frac{du_s}{dt} = -\frac{1}{R_1 C} \left( \frac{R_1}{R} u_s + U_{em} \cos \omega t \right)$$

$$\text{on a } \frac{R_1}{R} = 10 \Rightarrow \frac{R_1}{R} u_s < U_{em} \cos \omega t$$

(4)

$$\Rightarrow \frac{dus}{dt} = -\frac{U_{em}}{Rc} \cos \omega t$$

$$\Rightarrow us(t) = \int -\frac{U_{em}}{Rc} \cos \omega t dt$$

$$us(t) = -\frac{U_{em}}{Rc\omega} \sin \omega t + \frac{K}{\omega}$$

$U_e = 0$

$$u_c(0) = u_s(0) = 0$$

$$us(t) = -\frac{U_{em}}{Rc\omega} \sin \omega t$$

$$us(t) = \frac{-10}{10 \cdot 10^3 \times 100 \times 2\pi \times 10^3} \sin \omega t$$


$$us(t) = -1,59 \sin \omega t$$

2-4  $U_e = U_0 + U_{em} \cos \omega t$

on applique le théorème de superposition

$$us(t) = -\frac{R_1 U_0}{R} - \frac{U_{em}}{Rc\omega} \sin \omega t$$

$$us(t) = -2 - 1,59 \sin \omega t$$

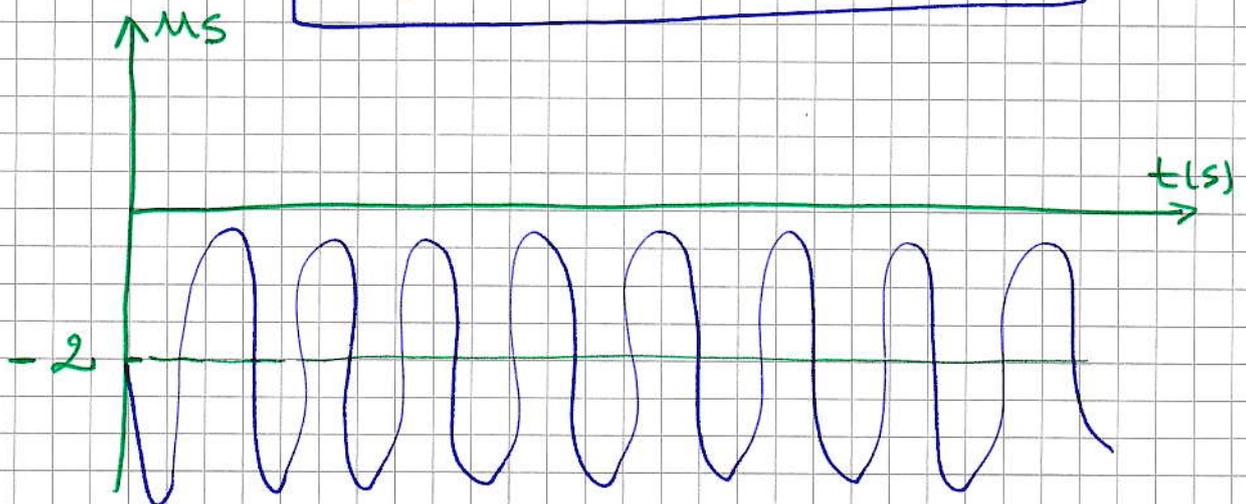

dans ce cas l'ALI ne polime pas.