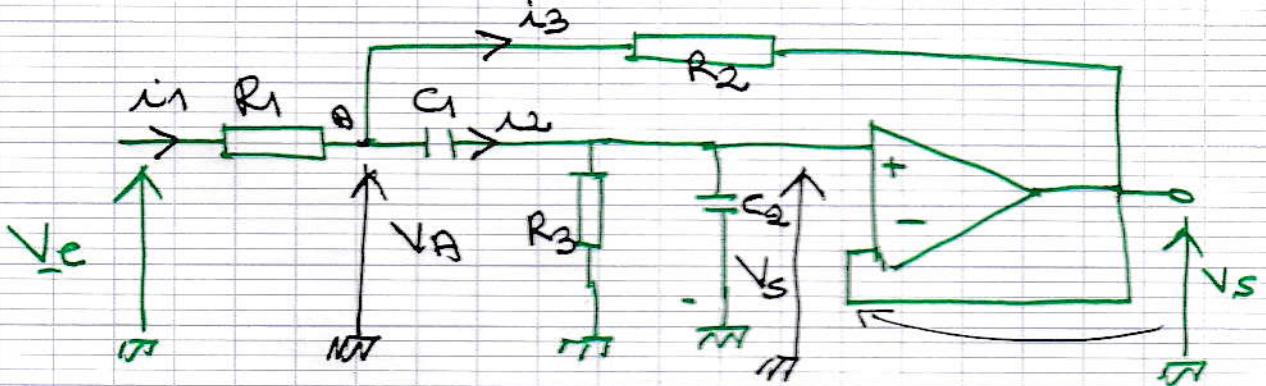


4

filtre passe bande




$$i_1 = \frac{V_A - V_s}{R_1}, \quad i_2 = \frac{V_A - V_s}{Z_{C_2}}$$

$$\text{et } i_3 = \frac{V_A - V_s}{R_2}$$

$$i_1 = i_2 + i_3$$
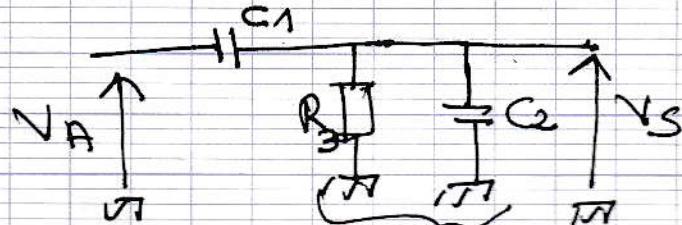
$$\frac{V_A - V_s}{R_1} = \frac{V_A - V_s}{Z_{C_1}} + \frac{V_A - V_s}{R_2} \quad (1)$$



$$Z'_1 = \frac{R_3 * Z_{C_2}}{R_3 + Z_{C_2}} = \frac{R_3 * \frac{1}{jC_2 \omega}}{R_3 + \frac{1}{jC_2 \omega}}$$

$$Z'_1 = \frac{R_3}{jC_2 \omega (R_3 + \frac{1}{jC_2 \omega})} = \frac{R_3}{1 + jR_3 C_2 \omega}$$

$$V_A = V_s \frac{\frac{Z'_1}{Z_{C_1} + Z'_1}}{1 + \frac{Z'_1}{Z_{C_1} + Z'_1}}$$

$$\Rightarrow V_A = V_s \left(\frac{Z_{C_1} + Z'_1}{Z'_1} \right) = V_s \left(1 + \frac{Z_{C_1}}{Z'_1} \right)$$

(5)

$$V_A = V_s \left(1 + \frac{Z_{C1}}{Z'} \right) \quad (2)$$

$$\textcircled{1} \rightarrow \frac{V_e}{R_1} = V_A \left(\frac{1}{R_1} + \frac{1}{Z_{C1}} + \frac{1}{R_2} \right) - V_s \left(\frac{1}{Z_{C1}} + \frac{1}{R_2} \right) \quad \textcircled{3}$$

(2) dann (3):

$$\frac{V_e}{R_1} = V_s \left(1 + \frac{Z_{C1}}{Z'} \right) \left(\frac{1}{R_1} + \frac{1}{Z_{C1}} + \frac{1}{R_2} \right) - V_s \left(\frac{1}{Z_{C1}} + \frac{1}{R_2} \right)$$

$$\frac{V_e}{R_1} = V_s \left[\frac{1}{R_1} + \frac{1}{Z_{C1}} + \frac{1}{R_2} + \frac{Z_{C1}}{Z' R_1} + \frac{1}{Z'} + \frac{Z_{C1}}{Z' R_2} \right] - \frac{1}{Z_{C1}} - \frac{1}{R_2}$$

$$\frac{V_e}{R_1} = V_s \left[\frac{1}{R_1} + \frac{Z_{C1}}{Z' R_1} + \frac{1}{Z'} + \frac{Z_{C1}}{Z' R_2} \right]$$

$$V_e = V_s R_1 \left[\frac{1}{R_1} + \frac{Z_{C1}}{Z'} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) + \frac{1}{Z'} \right]$$

$$V_e = V_s \left[1 + \frac{Z_{C1}}{Z'} \left(1 + \frac{R_1}{R_2} \right) + \frac{R_1}{Z'} \right]$$

$$T_2(j\omega) = \frac{V_s}{V_e} = \frac{1}{1 + \frac{Z_{C1}}{Z'} \left(1 + \frac{R_1}{R_2} \right) + \frac{R_1}{Z'}}$$

$$R_1 = R_2 = R_3 = 10k\Omega; C_1 = C_2 \approx 15nF$$

$$Z' = \frac{R}{1+jRC\omega}; Z_{C1} = \frac{1}{jC\omega}$$

$$T_2(j\omega) = \frac{1}{1 + \frac{1/jC\omega}{R} + 1 + \frac{R}{1+jRC\omega} + \frac{R}{1+jRC\omega}}$$

(6)

$$T_2(j\omega) = \frac{1}{1 + \frac{2(1+jRC\omega)}{jRC\omega} + 1 - jRC\omega}$$

$$T_2(j\omega) = \frac{1}{1 + \frac{2(1+jRC\omega)}{jRC\omega} + jRC\omega}$$

$$T_2(j\omega) = \frac{jRC\omega}{2jRC\omega + 1 + 2jRC\omega + jRC\omega}$$

$$T_2(j\omega) = \frac{jRC\omega}{2 + 4jRC\omega + (jRC\omega)^2}$$

$$T_2(j\omega) = \frac{1}{2} \times \frac{jRC\omega}{1 + 2jRC\omega + \frac{(jRC\omega)^2}{V^2}}$$

$$T_2(j\omega) = \frac{1}{2} \frac{jRC\omega}{1 + j\frac{2\sqrt{2}}{\sqrt{2}}\frac{\omega}{RC} + \left(\frac{j\omega}{\omega_0}\right)^2}$$

$$\omega_0 = \frac{\sqrt{2}}{RC}$$

$$T_2(j\omega) = \frac{1}{2} \frac{\sqrt{2}j \frac{\omega}{\sqrt{2}/RC}}{1 + j\frac{2\sqrt{2}\omega}{\omega_0} + \left(\frac{j\omega}{\omega_0}\right)^2}$$

$$T_2(j\omega) = \frac{1}{\sqrt{2}} \frac{j\omega/\omega_0}{1 + j\frac{2\sqrt{2}\omega}{\omega_0} + \left(\frac{j\omega}{\omega_0}\right)^2}$$

$$\boxed{\omega_0 = \frac{\sqrt{2}}{RC}} \quad \text{Let me calculate} \\ T(j\omega) = \underline{\underline{A(2j\omega/\omega_0)}}$$

$$\boxed{m = \sqrt{2}} \quad \boxed{A = 1/F} \quad \boxed{\omega_0 = \frac{\omega_0}{2\pi}} \\ \omega_0 = \frac{\sqrt{2}}{10 \cdot 10^3 \times 15159} = 9426.7 \text{ rad/s} \quad \omega_0 = \frac{\omega_0}{2\pi} \\ \omega_0 \approx 1500 \text{ Hz}$$