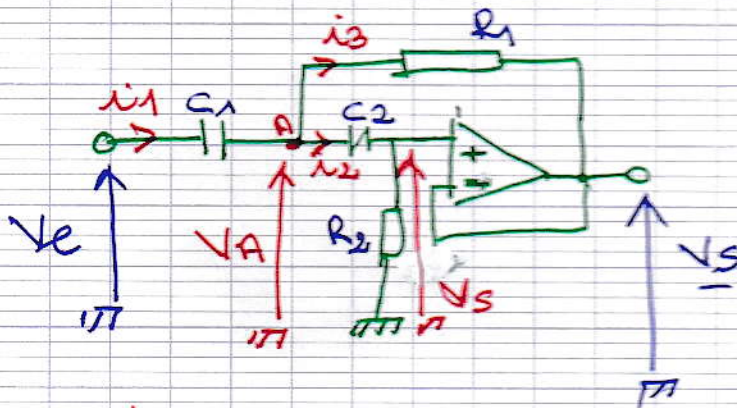


Correction TD. Filtré Sallen & Key



Filtré passe-haut

Loi des nœuds au pt A:

$$i_1 = i_2 + i_3$$


avec

$$\begin{cases} i_1 = \frac{V_e - V_A}{Z_{C1}} \\ i_2 = \frac{V_A - V_S}{Z_{C2}} \end{cases}$$

et $i_3 = \frac{V_A - V_S}{R_1}$

donc $\frac{V_e - V_A}{Z_{C1}} = \frac{V_A - V_S}{Z_{C2}} + \frac{V_A - V_S}{R_1}$

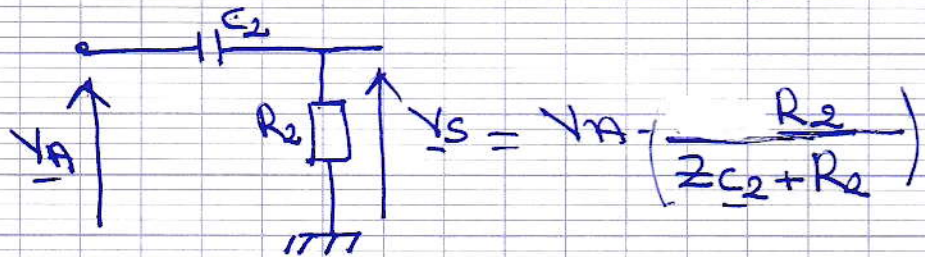① $\frac{V_e}{Z_{C1}} = V_A \left(\frac{1}{Z_{C1}} + \frac{1}{Z_{C2}} + \frac{1}{R_1} \right) - V_S \left(\frac{1}{Z_{C2}} + \frac{1}{R_1} \right)$



$$V_S = V_A \cdot \left(\frac{R_2}{Z_{C2} + R_2} \right)$$

$$\Rightarrow V_A = \frac{Z_{C2} + R_2}{R_2} V_S = \left(1 + \frac{Z_{C2}}{R_2} \right) V_S$$

$$\boxed{V_A = \left(1 + \frac{Z_{C2}}{R_2} \right) \cdot V_S} \quad \text{③}$$

③ dans ① \Rightarrow

$$\frac{V_e}{Z_{C1}} = \left(1 + \frac{Z_{C2}}{R_2} \right) V_S \times \left(\frac{1}{Z_{C1}} + \frac{1}{Z_{C2}} + \frac{1}{R_1} \right) - V_S \left(\frac{1}{Z_{C2}} + \frac{1}{R_1} \right)$$

(2)

$$\frac{V_e}{Z_{e1}} = V_s \left[\frac{1}{Z_{c1}} + \frac{1}{Z_{c2}} + \frac{1}{R_1} + \frac{Z_{c2}}{Z_{c1}R_2} + \frac{1}{R_2} + \frac{Z_{c2}}{R_1R_2} - \frac{1}{Z_{c2}} - \frac{1}{R_1} \right]$$

$$\frac{V_e}{Z_{e1}} = V_s \left[\frac{1}{Z_{c1}} + \frac{Z_{c2}}{Z_{c1}R_2} + \frac{1}{R_2} + \frac{Z_{c2}}{R_1R_2} \right]$$

$$T_1(j\omega) = \frac{V_s}{V_e} = \frac{1}{Z_{c1} \left[\frac{1}{Z_{c1}} + \frac{Z_{c2}}{Z_{c1}R_2} + \frac{1}{R_2} + \frac{Z_{c2}}{R_1R_2} \right]}$$

$$T_1(j\omega) = \frac{1}{1 + \frac{Z_{c2}}{R_2} + \frac{Z_{c1}}{R_2} + \frac{Z_{c1}Z_{c2}}{R_1R_2}}$$

$$T_1(j\omega) = \frac{1}{1 + \frac{Z_{c1} + Z_{c2}}{R_2} + \frac{Z_{c1}Z_{c2}}{R_1R_2}}$$

$$Z_{c1} = \frac{1}{j\omega C_1}; \quad Z_{c2} = \frac{1}{j\omega C_2}$$

$$T_1(j\omega) = \frac{1}{1 + \frac{1}{j\omega R_2 C_1} + \frac{1}{j\omega R_2 C_2} + \frac{1}{j^2 \omega^2 R_1 R_2 C_1 C_2}}$$

$$T_1(j\omega) = \frac{1}{1 + \frac{1}{j\omega R_2 C_1} + \frac{1}{j\omega R_2 C_2} + \frac{1}{j^2 \omega^2 R_1 R_2 C_1 C_2}}$$

$$T_1(j\omega) = \frac{1}{1 + \frac{1}{j\omega R_2} \left(\frac{1}{C_1} + \frac{1}{C_2} \right) + \frac{1}{j^2 \omega^2 R_1 R_2 C_1 C_2}}$$

③

$$R_1 = R_2 = R \text{ et } C_1 = C_2 = C$$

$$T_1(j\omega) = \frac{1}{1 + \frac{2}{jRC\omega} + \frac{1}{(jRC\omega)^2}}$$

$$T_1(j\omega) = \frac{(jRC\omega)^2}{(jRC\omega)^2 \left(1 + \frac{2}{jRC\omega} + \frac{1}{(jRC\omega)^2}\right)}$$

$$T_1(j\omega) = \frac{(j\frac{\omega}{\omega_0})^2}{(jRC\omega)^2 + 2jRC\omega + 1}$$

$$T_1(j\omega) = \frac{(j\frac{\omega}{\omega_0})^2}{1 + 2j\frac{\omega}{\omega_0} + (j\frac{\omega}{\omega_0})^2}$$

avec $\omega_0 = \frac{1}{RC}$

forme canonique d'un filtre passe haut
de 2nd ordre

$$T(j\omega) = \frac{A(j\frac{\omega}{\omega_0})^2}{1 + 2m j\frac{\omega}{\omega_0} + (j\frac{\omega}{\omega_0})^2}$$

$$2m = 2 \Rightarrow m = 1, A = 1$$

$$\omega_0 = \frac{1}{RC} = \frac{1}{10 \cdot 10^3 \times 10 \cdot 10^{-9}}$$

$$\omega_0 = 10^4 \text{ rad/s}$$

$$f_0 = \frac{\omega_0}{2\pi} = \underline{\underline{1590 \text{ Hz}}}$$