

①
correction:

[1]

$$P = U \cdot I \cdot \sqrt{3} \cos \varphi = 400 \times 10 \times \sqrt{3} \times 0,8$$

$$P = 5,542 \text{ kW}$$

puissance réactive:

$$Q = U \cdot I \cdot \sqrt{3} \sin \varphi = P \times \tan \varphi$$

$$\varphi = \cos^{-1}(0,8) = 36,86^\circ = 0,646 \text{ rad}$$

$$\text{donc } Q = 5,542 \times \tan 36,86 = 4,155 \text{ kvar}$$

$$Q = 4,155 \text{ kvar}$$

[2]

charge capacitive $\Rightarrow \varphi < 0$

$$\cos \varphi = 0,8 \Rightarrow \varphi = -\cos^{-1}(0,8) = -36,86^\circ$$

puissance active: $P = U \cdot I \cdot \sqrt{3} \cos \varphi = 400 \times 3 \times \sqrt{3} \times 0,8$

$$P = 1663 \text{ W}$$

puissance réactive: $Q = U \cdot I \cdot \sqrt{3} \sin \varphi = P \times \tan \varphi$

$$\text{avec } \varphi = -36,86^\circ$$

$$\text{donc } Q = 1663 \times \tan(-36,86) = -1247 \text{ var}$$

$$Q = -1247 \text{ var}$$

[3]

$$P = P_1 - P_2 = 115 + (-30) = \underline{85 \text{ W}}$$

[4]

$$Q = (P_1 - P_2) \times \sqrt{3} = (85 - 60) \times \sqrt{3}$$

$$Q = 44 \text{ var}$$

[5]

$$P = 3 \times 50 = 150 \text{ W}$$

[6]

$$P = 3 P_1 = 3 \times 50 = 150 \text{ W}$$

$$Q = 3 Q_1 = 3 \times (-15) = -45 \text{ var}$$

[7]

$$Q = P \times \tan \varphi \Rightarrow P = \frac{Q}{\tan \varphi}; \varphi = \cos^{-1}(0,8)$$

$$P = 500 / \tan(\cos^{-1}(0,8)) = \underline{667 \text{ W}}$$

(2)

8)

$$I_n = \frac{S_n}{U_n \sqrt{3}} = \frac{1000}{400 \times \sqrt{3}} = 1,45 \text{ A}$$

9)

$$S = \sqrt{P^2 + Q^2} = \sqrt{8^2 + 6^2} = 10 \text{ kVA}$$

10)

$$P_J = \frac{3}{2} R_m I^2 = \frac{3}{2} \times 1,5 \times 10^2 = 225 \text{ W}$$

11)

$$1) \underline{Z} = \underline{Z}_R + \underline{Z}_L = R + jL\omega$$

2°)

$$Z = \sqrt{R^2 + (L\omega)^2} = \sqrt{100^2 + (0,1 \times 314)^2}$$

$$\underline{Z} = 104,8 \Omega$$

$$(Z_L = 0,1 \times 314 = 31,4 \Omega)$$

3°)

$$\varphi = \tan^{-1} \left(\frac{Z_L}{Z_R} \right) = \tan^{-1} \left(\frac{31,4}{100} \right) = 0,304 \text{ rad}$$

$$\underline{\varphi} = 17,34^\circ$$

l'angle φ représente le déphasage entre le courant de phase $\vec{I}$ et la tension $\vec{U}$ comparés.

$$\varphi = (\vec{I}_{12}, \vec{U}_{12}) = (\vec{I}_{23}, \vec{U}_{23}) = (\vec{I}_{31}, \vec{U}_{31})$$

4°)

$$I = \frac{U}{Z} = \frac{230}{104,8} \approx 2,2 \text{ A}$$

5°)

$$I_n = I \times \sqrt{3} = 2,2 \times \sqrt{3} = 3,80 \text{ A}$$

6°)

$$\cos \varphi = \cos(17,34^\circ) = 0,954$$

7°)

$$P = U \cdot I \cdot \sqrt{3} \times \cos \varphi \text{ et } Q = U \cdot I \cdot \sqrt{3} \times \sin \varphi$$

8°)

$$P = 230 \times 3,8 \times \sqrt{3} \times 0,954 = 1444 \text{ W}$$

$$Q = P \times \tan \varphi = 1444 \times \tan(17,34^\circ) = 453 \text{ Var}$$

9°)

$\varphi > 0$ aussi $Q > 0 \Rightarrow$ le récepteur est de nature inductif.

31

12

1°) $P_1 = U \times J \times \cos \varphi$

2°) $Q_1 = U \times J \times \sin \varphi$

3°) $P = 3 \times P_1$

4°) $Q = 3 \times Q_1$

5°) a) $J = \frac{U}{Z} = \frac{400}{10+18} = 3,82 \text{ A}$


b) $P_1 = 400 \times 3,82 \times \cos(17,14) = 1458 \text{ W}$

$Q_1 = 400 \times 3,82 \times \sin(17,14) = 458 \text{ Var}$

c) $P = 3 \times P_1 = 3 \times 1458 = 4,374 \text{ kW}$

$Q = 3 \times Q_1 = 3 \times 458 = 1,374 \text{ kVar}$

13

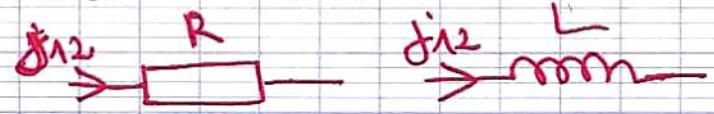

1°) $P_1 = R J^2$

2°) $P_L = 0 \text{ W}$ | Non elle ne consomme pas
 $P_L = U_L \times J \cos \varphi_L = 0 \text{ car } \cos 90^\circ = 0$

3°) $Q_L = Z_L \times J^2 = L \omega J^2$

4°) $Q_R = 0 \text{ car } Q_L = U J \sin \varphi_L = 0 \text{ Var}$

5°) a) $P_R = 100 \times 3,82^2 = 1444 \text{ W}$

$Q_L = Z_L J^2 = 31,4 \times 3,82^2 = 454 \text{ Var}$

b) $Q = 3 P_R = 3 \times 1444 = 4332 \text{ W}$

$Q = 3 Q_L = 3 \times 454 = 1362 \text{ Var}$